

## Chapter 1

Slide 17:

$$A_v = 100 \text{ V/V}$$

$$\begin{aligned} A_v \text{ in dB} &= 20 \log_{10} A_v \\ &= 20 \log_{10} 100 \\ &= 20 \log_{10} 10^2 \\ &= 2 \times 20 \\ &= 40 \text{ dB} \end{aligned}$$

$$A_v = 1000 \text{ V/V}$$

$$\begin{aligned} A_v \text{ in dB} &= 20 \log_{10} A_v \\ &= 20 \log_{10} 10^3 \\ &= 3 \times 20 \\ &= 60 \text{ dB} \end{aligned}$$


Or you can use calculator

$$A_v = 10K \text{ V/V}$$

$$\begin{aligned} A_v \text{ in dB} &= 20 \log_{10} 10^4 \\ &= 20 \times 4 \\ &= 80 \text{ dB} \end{aligned}$$

## Slide 20:

From the information in the question,

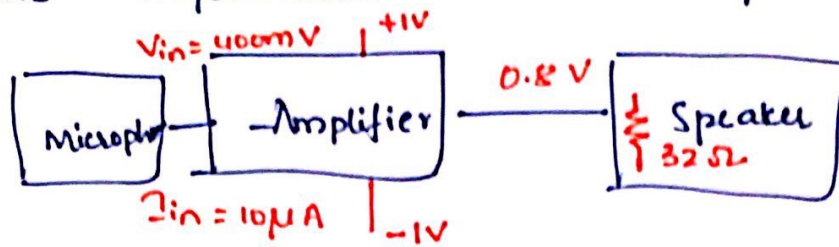

$$V_{in} = 400\text{mV}$$

$$V_{out} = 0.8\text{V}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{0.8}{0.4} = 2\text{ V/V}$$

$$R_L = 32\Omega$$

$$A_v \text{ in dB} = 20 \log_{10} 2 = 6\text{ dB}$$

$$I_{out} = V_{out} / R_L = \frac{0.8}{32} = 25\mu\text{A}$$

$$I_{in} = 10\mu\text{A}$$

$$A_i = \frac{I_{out}}{I_{in}} = \frac{25\mu}{10\mu} = 2.5\text{ A/A}$$

$$A_i \text{ in dB} = 7.9\text{ dB}$$

$$\text{Power gain} = \frac{P_{out}}{P_{in}} = \frac{V_{out} \cdot I_{out}}{V_{in} \cdot I_{in}}$$

$$= \left( \frac{V_{out}}{V_{in}} \right) \left( \frac{I_{out}}{I_{in}} \right)$$

$$= A_v \cdot A_i$$

$$= 2 \times 2.5 = 5\text{ W/W}$$

$$10 \log_{10} 5 = 6.98\text{ dB}$$

$$\text{Power gain in dB} = 20 \log_{10} 5 = 13.97\text{ dB}$$

$$\text{or } \boxed{A_i \text{ dB} + A_v \text{ dB}} = 13.9\text{ dB}$$

$$\frac{1}{2} [A_i \text{ dB} + A_v \text{ dB}] = \frac{1}{2} [6 + 7.9]$$

$$= \frac{13.9}{2}$$

$$= 6.9\text{ dB}$$

Slide 23:


$$i_c(t) = I_c + i_c(t)$$

$i_c(t)$  — Total current

$I_c$  — DC current

$i_c(t)$  — AC current

Slide 25:

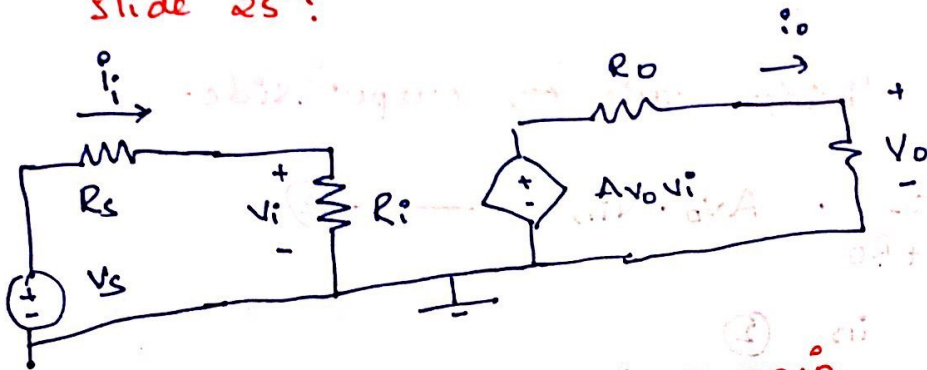

$A_{v0}$  — open loop gain

$A_v$  — closed loop gain

open loop gain —  $A_{v0}$  — when you buy an amplifier, you will get the amplifier with some gain that you can find in the datasheet.


closed loop gain —  $A_v$  — Gain of the amplifier after you add source and load.

$$A_v = \frac{V_o}{V_s}$$

On

Relation between openloop gain and closed loop gain:

$$A_v = \frac{V_{out}}{V_s}$$

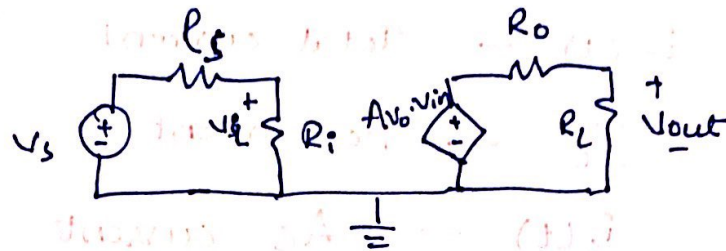

Apply voltage divider rule on input side.

$$V_i = \frac{R_i}{R_i + R_s} \cdot V_s \quad \text{--- (1)}$$

Apply voltage divider rule on output side.

$$V_{out} = \frac{R_L}{R_L + R_o} \cdot A_{v0} \cdot V_i \quad \text{--- (2)}$$

Substitute (1) in (2)


$$V_{out} = \frac{R_L}{R_L + R_o} \cdot A_{v0} \cdot \frac{R_i}{R_i + R_s} \cdot V_s$$

$$A_v = \frac{V_{out}}{V_s}$$

$$\frac{V_{out}}{V_s} = A_v = \underbrace{\frac{R_L}{R_L + R_o} \cdot \frac{R_i}{R_i + R_s} \cdot A_{v0}}_{\text{closed loop gain}} \quad \text{--- open loop gain}$$

Slide 27:


Input Resistance:

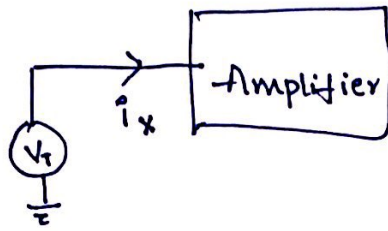

Apply a known voltage source and measure current

$$R_i = \frac{V_T}{i_x}$$

Output Resistance:

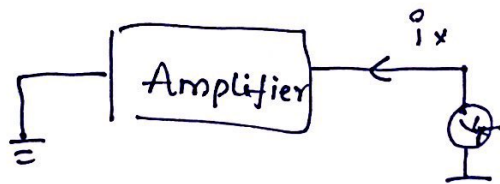

eliminate input source

Apply a known voltage source at the output and measure current

$$R_o = \frac{V_T}{i_x}$$